

# Boolean Algebra and Logic Gates

## Part 1: Boolean Algebra

Boolean algebra originates from George Boole, 19<sup>th</sup> Century British mathematician and philosopher — see excerpt from his Laws of Thought on resources page.

Boolean algebra deals with 2 states: true, false  
on, off  
1, 0

Boolean variable: variable that can take one of two values (typically 0 or 1).

Boolean function: — inputs are one or more Boolean variables.  
— output is a single Boolean variable.

[Why are we interested? Because this is all computers do, all day every day!!]

Can define a Boolean function by a truth table

e.g.  $f(a, b)$  defined by

a	b	$f(a, b)$
0	0	0
0	1	1
1	0	0
1	1	0

e.g.  $g(a,b,c)$  defined by

a	b	c	$g(a,b,c)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Elementary Boolean functions include:

AND

a	b	a AND b
0	0	0
0	1	0
1	0	0
1	1	1

OR

a	b	a OR b
0	0	0
0	1	1
1	0	1
1	1	1

NOT

a	NOT a
0	1
1	0

Notation varies quite a bit:

$$\begin{array}{l}
 a \text{ AND } b \equiv ab \\
 a \text{ OR } b \equiv a + b \\
 \text{NOT } a \equiv \bar{a}
 \end{array}
 \equiv a \cdot b \equiv a \wedge b \equiv a \&\& b \\
 \equiv a' \equiv \neg a \equiv a \vee b \equiv a \parallel b \\
 \equiv \neg a \equiv !a$$

*architecture text book*      *AI text book*      *Java*

some logic books even use  $a+b$  for  $a$  AND  $b$ !  
BEWARE!!

We can combine elementary Boolean functions to get any Boolean function

e.g.  $\bar{a}b$ :

a	b	$\bar{a}$	$\bar{a}b$
0	0	1	0
0	1	1	1
1	0	0	0
1	1	0	0

looking back, we see  $f(a, b) = \bar{a}b$ .

# [ Demo TruthTable.java ]

Activity: Consider the Boolean function  $c\bar{a}\bar{b} + a\bar{b}\bar{c}$

- ① work out the truth table by hand
- ② check using TruthTable.java
- ③ look back - is this function the same as one we've seen already?

optional:

④ try  $\bar{b} (c\bar{a} + a\bar{c})$

is this the same as something we've seen?


→ important point: same function can be represented by different formulas

e.g.  $\bar{b} (c\bar{a} + a\bar{c}) = c\bar{a}\bar{b} + a\bar{b}\bar{c}$


# Part 2: Logic Gates

- Computer circuits are built out of gates that implement simple Boolean functions.
- A gate is built from a few transistors.
- Common gates and their circuit symbols are:


AND

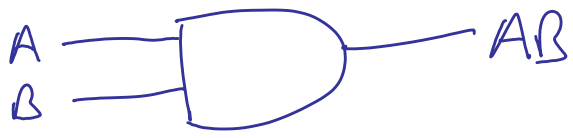

OR

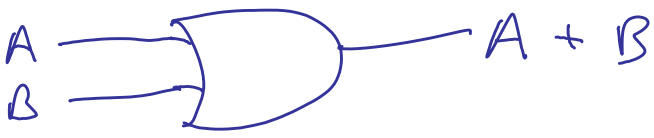


NOT

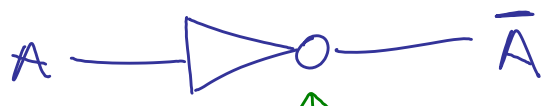


sometimes this "O" represents a NOT attached to another gate

XOR

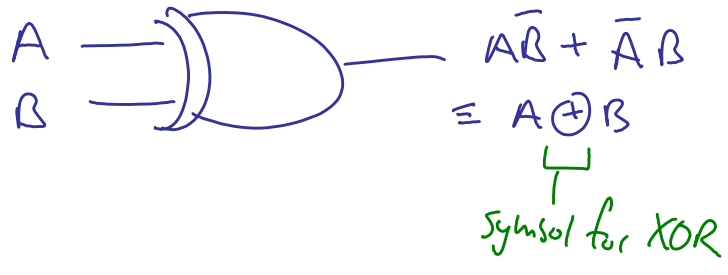


A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0



NAND

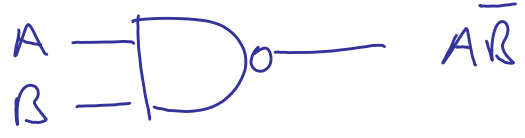

NOR

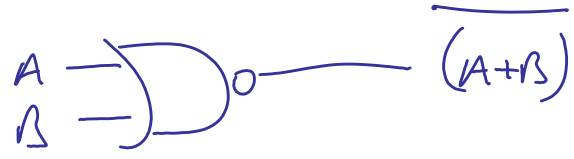


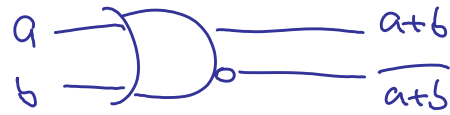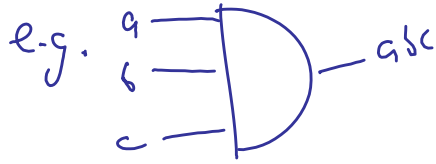- NAND is a universal gate i.e. you can build all others from it
- NOR is also universal.
- gates can have multiple inputs or outputs



- Any Boolean function can be implemented using a combination of gates

e.g.  $f(x, y, z) = x + \bar{y}z$

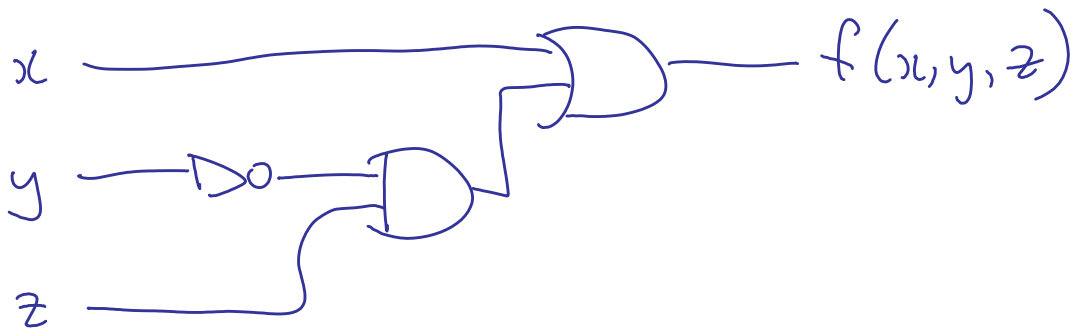

ACTIVITY: build  $f$  using SimCircuit.